



**Green University of Bangladesh**  
**Department of Computer Science and Engineering (CSE)**  
**Faculty of Sciences and Engineering**  
**Semester:( Spring, Year:2024), B.Sc. in CSE (Day)**

**Lab Report NO:**  
**Course Title: Digital Logic Design Lab**  
**Course Code: CSE 204 Section: 231-D1**

**Lab Experiment Name: Verification of truth tables of the basic Flip-Flops  
with synchronous and asynchronous modes.**

**Student Details**

Name		ID
1.	Promod Chandra Das	231002005

**Lab Date** :  
**Submission Date** :  
**Course Teacher's Name** : **Md. Shihab Hossain**

**Lab Report Status**


**Marks:** .....

**Comments:**.....


**Signature:**.....

**Date:**.....

 
➤ Implement D flip-flop and verify with truth table



Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

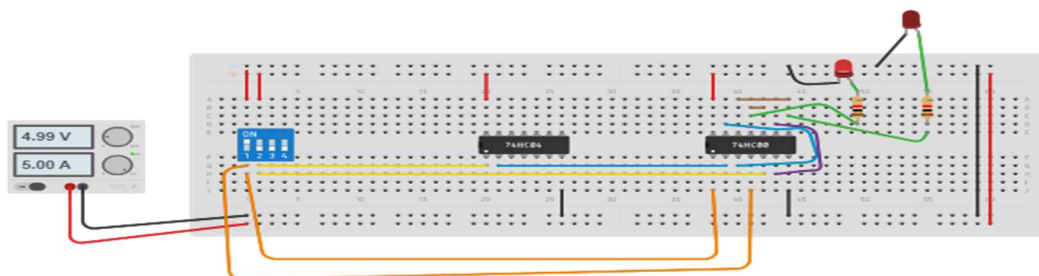

 ➤ Implement T flip-flop and verify with truth table



T flip-flop

T	Clock	Q	Q'
0	↑	Q	Q'
1	↑	Q'	Q
X	↓	Q	Q'

